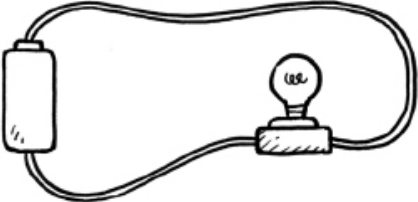


## Circuits and bulbs

- Set up each circuit as shown below. Write a sentence under each picture to describe what happens in the circuit. Try to compare it with other circuits.
  - Can you see any pattern in the results? Can you explain this pattern?
- Write your answer on the back of this sheet.




1. One battery and one bulb

---



---

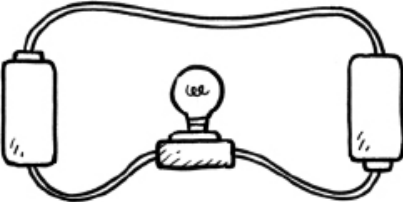


2. Two batteries and one bulb

---



---

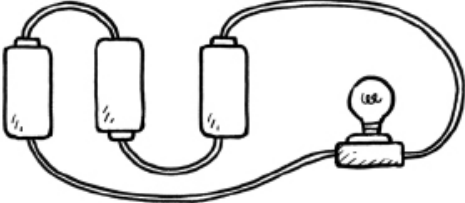


3. Three batteries and one bulb

---



---

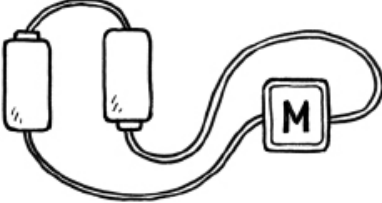


4. Two batteries and one motor

---



---

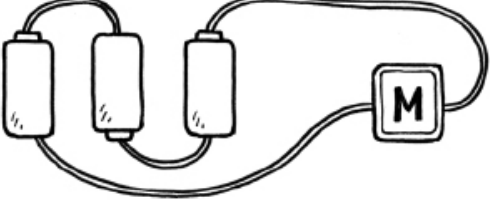


5. Three batteries and one motor

---



---

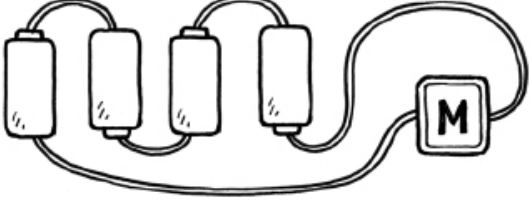

6. Four batteries and one motor

---



---

I can make circuits containing different numbers of components and explain what happens.

How did you do? 